

Solutions for EE461 Midterm Exam 2 26/5/21

1- Considering the following equations that are used in DC machines,

$$T = K\phi I_a, \quad E_g = K\phi \omega$$

$$\omega \text{ rad/sec} \Rightarrow K\phi = \frac{\text{V.sec}}{\text{rad}}$$

In question 1, $K\phi = 0.042 \text{ V/rpm}$

0.042 V/rpm is converted to $\frac{\text{V.sec}}{\text{rad}}$ as,

$$\frac{30}{\pi} \times 0.042 = 0.45 \frac{\text{V.sec}}{\text{rad}}$$

Therefore, $K\phi = 0.45$ will be used in solving the problem.

a) At no-load (when the rotational losses are neglected) $\Rightarrow I_a = 0$

$$KV_d = RaI_a + E_g = 1.2 \times 0 + E_g = 120$$

$$K\phi \omega = 120 \Rightarrow \omega = \frac{120}{0.45} = 300 \text{ rad/sec}$$

$$n = \omega \times \frac{30}{\pi} = 2865 \text{ rpm}$$


At the time of starting $n = w = 0 \Rightarrow E_g = 0$

$$KV_d = RaI_a + 0 \Rightarrow I_{ast} = \frac{1 \times 120}{1.2} = 100 \text{ A}$$

$$T = K\phi I_a = 0.4 \times 100 = 40 \text{ A}$$

$$b - n(T=0) = 2865 \text{ rpm}$$

$$T(n=0) = 40 \text{ N.m.}$$

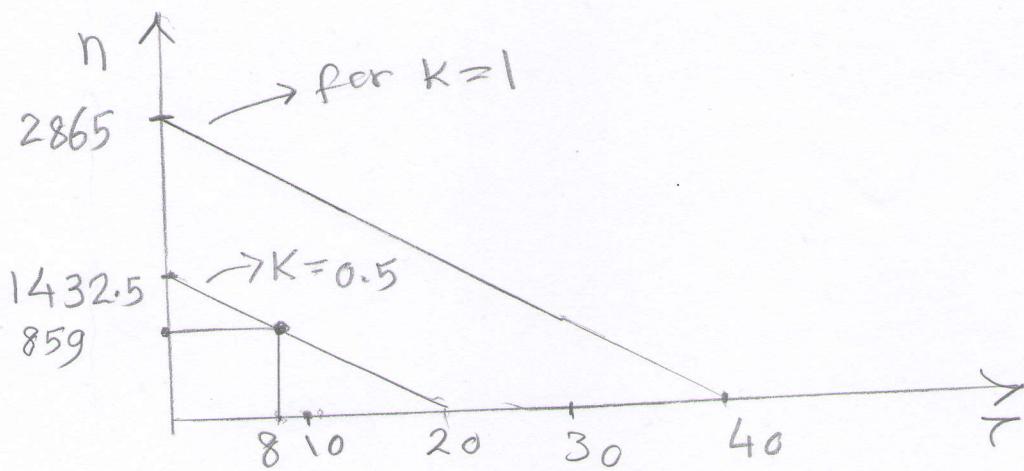

$$c - KV_d = R_a I_a + K\phi \omega$$


$$0.5 \times 120 = 1.2 \times \frac{T}{K\phi} + K\phi \omega$$

$$60 = 1.2 \times \frac{8}{0.4} + 0.4 \omega \Rightarrow \omega = 90 \text{ rad/sec}$$

$$n = 90 \times \frac{30}{\pi} = 859 \text{ rpm}$$

2-

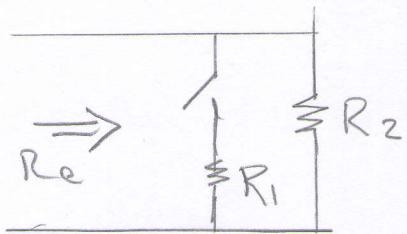Firstly, We derive the equivalent resistance



During on state the input resistance = $R_1 \parallel R_2$

$$\text{During off state} \quad " \quad " \quad " \quad " = R_2$$

$$\Rightarrow R_e = K R_1 \parallel R_2 + (1-K) R_2 = \frac{K R_1 R_2}{R_1 + R_2} + \frac{(1-K) R_2}{1}$$

$$R_e = \frac{K R_1 R_2 + R_1 R_2 + R_2^2 - K R_1 R_2 - K R_2^2}{R_1 + R_2}$$

$$R_e = \frac{R_2^2 (1-K) + R_1 R_2}{R_1 + R_2}$$

a) $\omega_m = 850 \times \frac{\pi}{30} = 89 \text{ rad/sec}$

$$T_L = 780 \left(\frac{850}{1200} \right)^2 = 391.17 \text{ N.m}$$

$$\omega_s = 2 \times 377 / 4 = 188.5$$

$$I_d = \frac{T_L \omega_s}{2.3394 V_s n_m}$$

$$I_d = \frac{391.17 \times 188.5}{2.3394 \times 275.8 \times 0.95} = 120.65 \text{ A}$$

$$\omega_m = \omega_s (1-s) = \omega_s \left[1 - \frac{I_d R_e}{2.3394 V_s n_m} \right]$$

$$s = \frac{I_d R_e}{2.3394 V_s n_m}$$

3/4

89 The speed is min when $K = 0$
 (switch is open circuit)

$$89 = 188.56 \left(1 - \frac{124.93 R_2}{2.3394 \times 275 \times 0.95} \right)$$

$$\Rightarrow R_2 = 2.5823 \Omega$$

b)

$$\text{At } n_m = 1100$$

$$T_L = 780 \left(\frac{1100}{1200} \right)^2 = 655.42 \text{ N.m}$$

$$I_d = \frac{655.42 \times 188.5}{2.3394 \times 275 \times 0.95} = 2202.15$$

$$c) \omega_m = \frac{1100 \times \pi}{30} = 115.19 \text{ rad/sec}$$

$$115.19 = 188.5 \left[1 - \frac{209.32 \times R_e}{2.3394 \times 275 \times 0.95} \right]$$

$$R_e = 1.136 \Omega$$

$$1.136 = \frac{2.5823^2 (1-K) + 0.01 \times 2.5823}{0.01 + 2.5823}$$

$$K = 0.5623$$